

Bachelor of Technology
in
Electronics and Communication Engineering by

Name: - Arpit Jain
Roll No: 23UEC523

Course Coordinator
Dr. Nikhil Raj



Topic: -Implement a frequency divider using T flip-flops, where the input clock frequency is divided by 2^N , with N being the number of flip-flops

Department of Electronics and Communication Engineering The LNM
Institute of Information Technology, Jaipur

November 2024

Copyright © The LNMIIT 2024 All
Rights Reserved

CONTENTS

TOPIC	PAGE NO
1. AIM OF THE PROJECT	3
2. INTRODUCTION	3
3. CODE OF THE PROJECT	4
4. SCHEMATIC DIAGRAM	5
5. SIMULATION TIMING DIAGRAM	6
6. PROJECT SUMMARY	7
7. CONSTRAINT FILE	8
8. FPGA BOARD IMPLEMENTATION	8
9. SUMMARY	9

AIM OF THE PROJECT :-

Implement a frequency divider using T flip-flops, where the input clock frequency is divided by 2^N , with N being the number of flip-flops.

INTRODUCTION :-

What is T Flip Flop ?

- T flip flop or to be more precise is known as Toggle Flip Flop because it is capable of toggling its output based on the input.
- T there, stands for Toggle.
- Toggle basically means that the bit will flip that is either from 1 to 0 or from 0 to 1.

In this design we are using T Flip Flops to divide the input clock frequency by 2, and every subsequent division is performed by another T flip flop in series.

If we chain together in series, two T-type flip-flops the input frequency first will get "divided-by-two" by the first flip-flop $f \div 2$ and then "divided-by-two" again by the second flip-flop $\div 2$, giving an output frequency which has effectively been divided four times, then its output frequency becomes one quarter value 25% of the original clock frequency, ($f \div 4$).

Each time we add yet another toggle or "T-type" flip-flop to the chain, the output clock frequency is halved or divided-by-2 again and so on, giving an output frequency of 2^n where "n" is the number of flip-flops used in the sequence. The T flip flop requires 2 clock cycle for toggling 1 for high and other for low. That's why this property of toggling of T flip flops helps to divide frequency by factor of 2.

So we can now see that the output from the T-type flip-flop is at half the frequency of the input, in other words it counts in 2's. By cascading together more Toggle FlipFlops, we can produce a divide-by-2, divide-by-4, divideby-8, etc. circuit which will divide the input clock :-frequency by 2, 4 or 8 times, in fact any value to the powerof2 we want making a binary counter circuit.

CODE FOR THE PROJECT :-

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FrequencyDivider is  Generic (N : integer := 3);
  Port ( clk : in STD_LOGIC;
        T  : in STD_LOGIC;
        Y  : inout STD_LOGIC_VECTOR(N-1 downto 0) := (others => '0'));
end FrequencyDivider;

architecture Behavioral of FrequencyDivider is  signal Q :
STD_LOGIC_VECTOR(N-1 downto 0) := (others => '0'); begin

  process(clk,T)  begin
    if rising_edge(clk) then
      if T = '1' then
        Q(0) <= not Q(0); -- First flip-flop toggles with each clock pulse
        for i in 1 to N-1 loop
          Q(i) <= Q(i) xor Q(i-1);
        end loop;
      end if;
    end if;
  end process;
  Y <= Q;

end Behavioral;
```

SCHEMATIC DIAGRAM :-

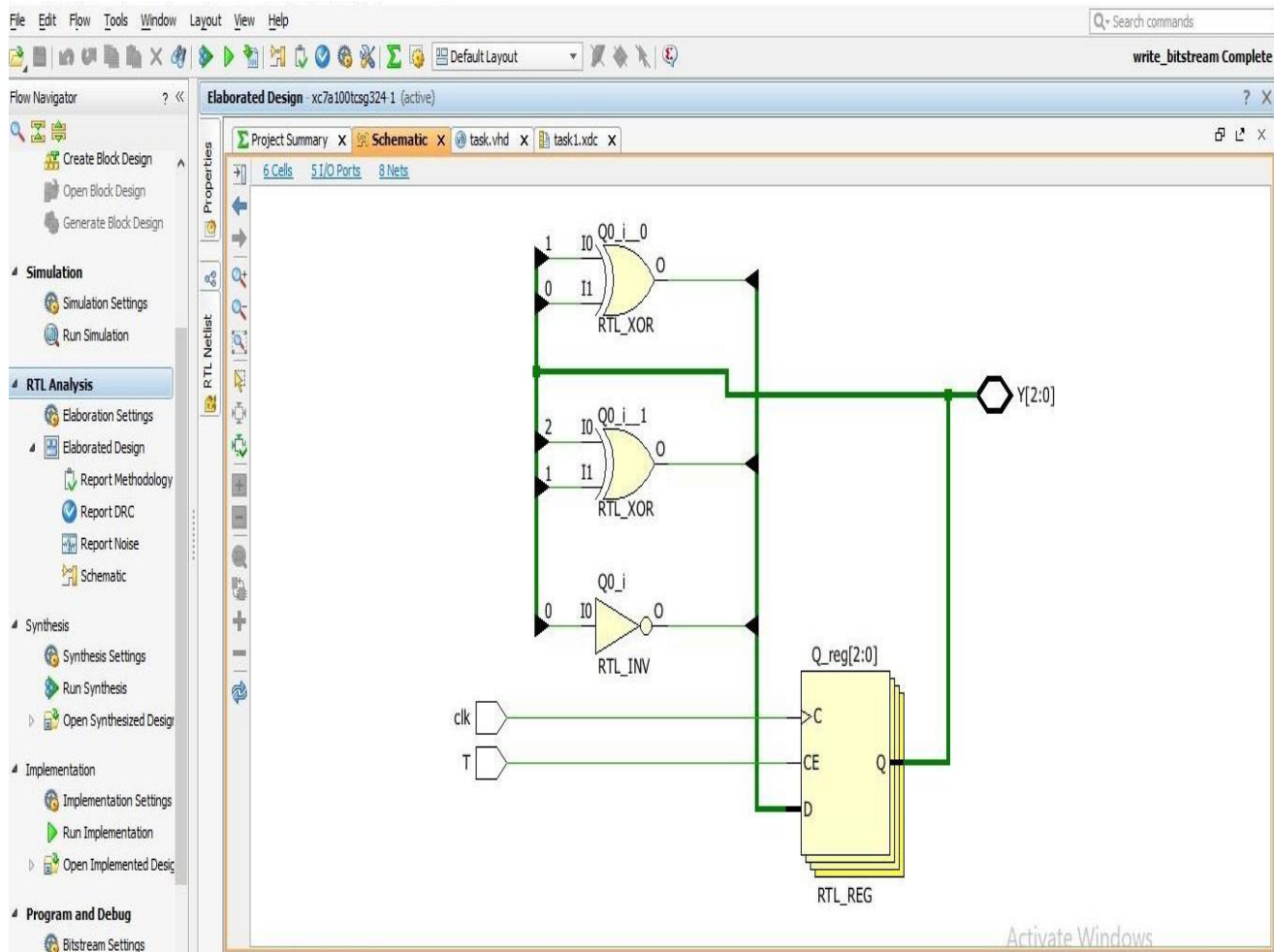


FIGURE 1 : Schematic diagram for frequency divider using T flip flops

SIMULATION TIMING DIAGRAM :-

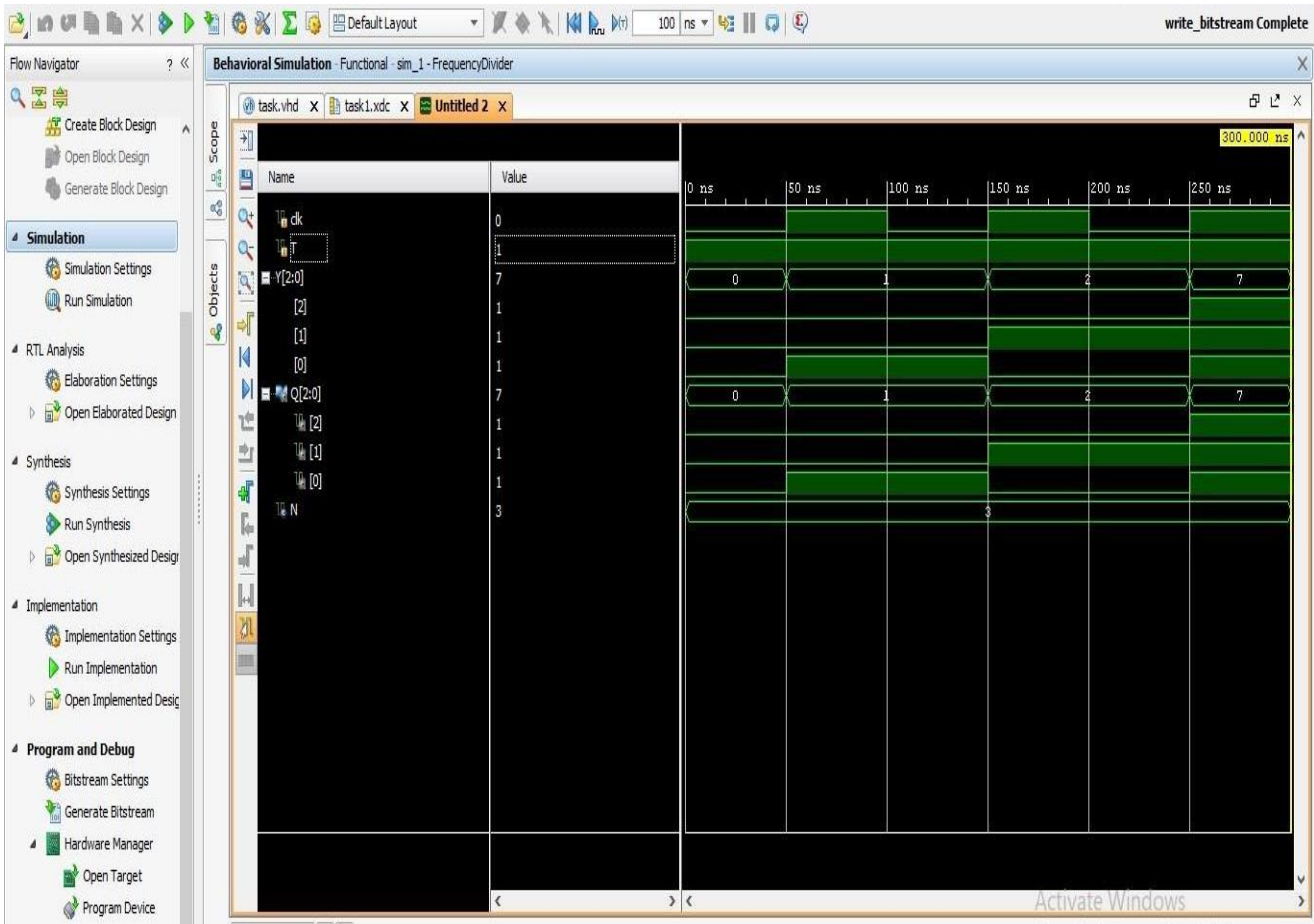


FIGURE 2 Simulation diagram for frequency divider using T flip flops

Project Summary:

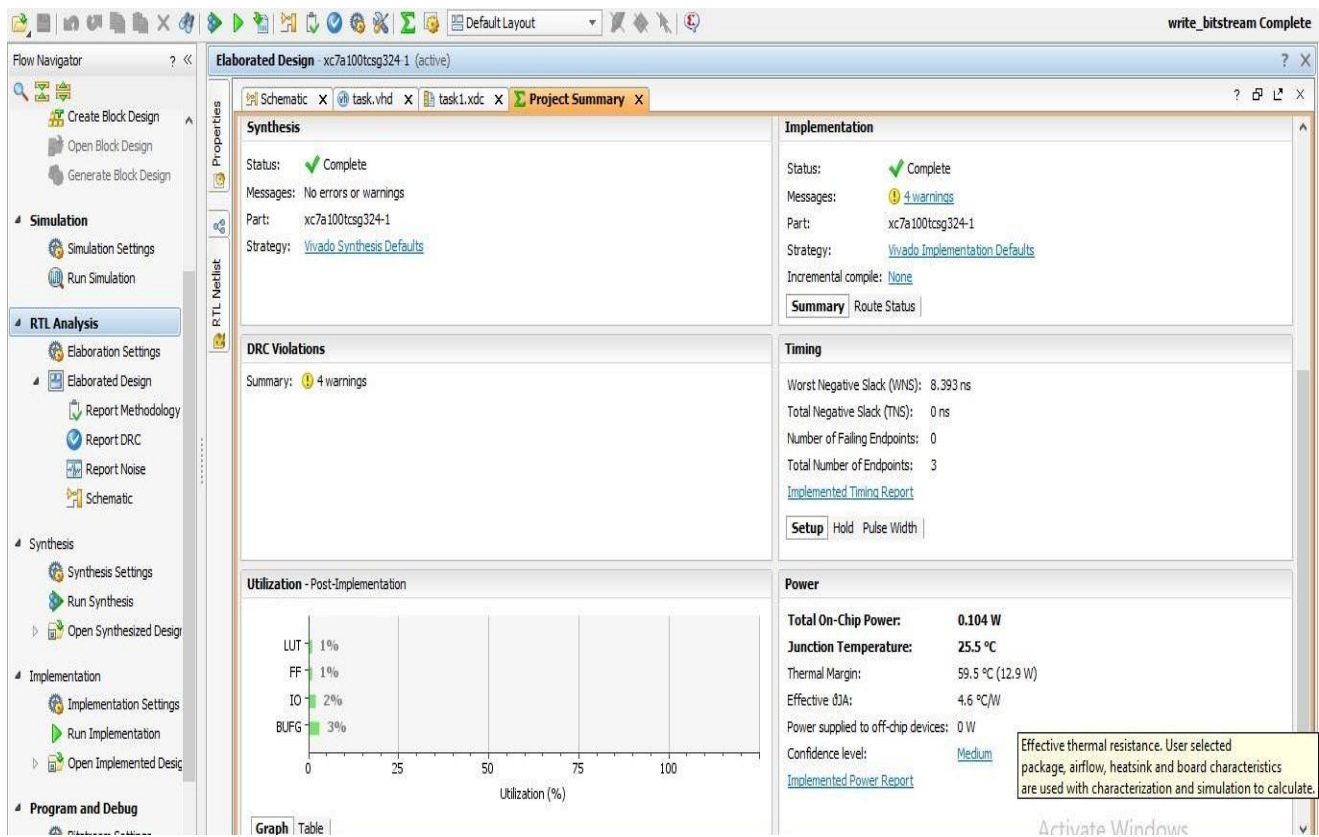


Figure 3 Project summary for frequency divider using T flip flops

CONSTRAINT FILE :-

```
## Clock signal set_property -dict { PACKAGE_PIN E3  IOSTANDARD LVCMOS33 }
[get_ports {clk }];
```

```
#IO_L12P_T1_MRCC_35 Sch=clk100mhz
```

```
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {clk }];
```

```
##Switches set_property -dict { PACKAGE_PIN J15  IOSTANDARD LVCMOS33 } [get_ports { T}]; #IO_L24N_T3_RS0_15 Sch=sw[0]
```

LEDs

```
set_property -dict { PACKAGE_PIN K15  IOSTANDARD LVCMOS33 } [get_ports { Y[0] }]; #IO_L24P_T3_RS1_15 Sch=led[1]
```

```
set_property -dict { PACKAGE_PIN J13  IOSTANDARD LVCMOS33 } [get_ports { Y[1] }];
```

```
#IO_L17N_T2_A25_15 Sch=led[2] set_property -dict { PACKAGE_PIN N14 IOSTANDARD LVCMOS33 } [get_ports { Y[2] }]; #IO_L8P_T1_D11_14 Sch=led[3]
```

FPGA BOARD IMPLEMENTATION :-



FIGURE 4

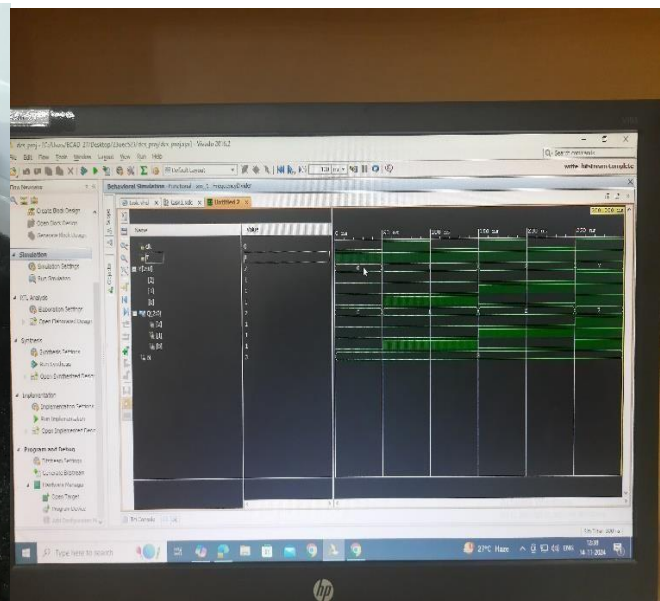


FIGURE 5

SUMMARY :-

In this project, a frequency divider was successfully designed and implemented using (N=3) T flip-flops to reduce the input clock frequency by 2^N . The design leveraged the toggling behavior of T flip-flops, where the cascading arrangement allowed progressive division of the clock frequency.

The VHDL implementation demonstrated the flexibility and scalability of the design as shown by the parameterized N, which made the design applicable to any divisor factor. The circuit was functional efficiently to give a stable output clock signal satisfying several demands of digital systems.

This frequency divider serves as a fundamental building block in applications requiring clock management, timing control, or frequency synthesis. The project highlights the simplicity and versatility of using T flip-flops for frequency division, making it a valuable contribution to digital circuit design.

We use FPGA(Field-Programmable Gate Array) to implement the frequency divider circuit. We can configure and reconfigure the device as much as we want. At every input we can generate bitstream according to code and implement that on board.